



Casa abierta al tiempo

ARQUITECTURA MIPS EN VHDL

Arquitectura de Computadoras

Esaú Acosta Lara

2153036850



Casa abierta al tiempo

**UNIVERSIDAD AUTÓNOMA METROPOLITANA
AZCAPOTZALCO**

CBI DIVISIÓN DE
CIENCIAS BÁSICAS
E INGENIERÍA
UAM - Azcapotzalco

INTRODUCCIÓN

John L. Hennessy, junto con su equipo, en la Universidad de Stanford comenzó a trabajar en lo que es el primer procesador MIPS. El concepto básico era para aumentar el rendimiento mediante el uso de tuberías de instrucciones profundas. Canalización como "la ciencia básica" era muy conocida antes, pero no se convirtió en su potencial máximo. Las CPU se construyen a partir de una serie de subunidades dedicadas como decodificadores de instrucciones, ALU, unidades de carga / almacenamiento, etc. En un diseño no optimizado tradicional, una instrucción particular en una secuencia del programa debe estar listo antes de la próxima puede ser emitida para su ejecución, en una arquitectura segmentada, las instrucciones sucesivas son posibles suponer en la ejecución.

Un aspecto importante del diseño de MIPS era para adaptarse a cada sub-fase, cuentos como memoria caché de acceso, de todas las instrucciones en un ciclo, eliminación de esta herramienta para cualquier necesidad de enclavamiento, y que permitía un solo ciclo de rendimiento.

En otros aspectos el diseño MIPS fue en gran medida un típico diseño RISC. Para guardar los bits de la palabra de instrucción, diseños RISC reducir el número de instrucciones para codificar. El diseño MIPS usa 6 bits de la palabra de 32 bits para el código de operación básico, y el resto puede contener una dirección de salto solo 26 bits o puede tener hasta cuatro campos de 5 bits que especifica hasta tres registros además de un valor de cambio combinado con otros 6 bits de código de operación; Otro formato, entre varios, específico dos registros combinados con un valor inmediato de 16 bits, etc. Esto permite que esta CPU para cargar hasta la instrucción y los datos que se necesitan en un solo ciclo, mientras que no lo sea RISC, tales como el MOS Technology 6502, por ejemplo, requiere ciclos separados para cargar el código de operación y los datos. Esta fue una de las mejoras de rendimiento importante que RISC ofrece. Sin embargo, los diseños modernos de no-RISC logran esta velocidad por otros medios

MIPS (microprocesador sin etapas de interconexión de tuberías; microprocesador sin bloqueos en las etapas de segmentación) es una arquitectura diseñada para optimizar la segmentación en unidades de control y para facilitar la generación automática de código máquina por parte de los compiladores. Existen múltiples revisiones del conjunto de instrucciones MIPS:






Versión	Ancho de los registros	Procesadores	Comentarios
MIPS I	32	R2000, R3000	Versión comercial del procesador MIPS de la Universidad de Stanford
MIPS II	32	R6000	Base del estándar MIPS32
MIPS III	64	R4000	Primera arquitectura MIPS de 64 bits
MIPS IV	64	R5000, R10000	Actualización menor de MIPS III
MIPS V	64	-	Base del estándar MIPS64

Implementaciones MIPS se usa principalmente en sistemas embebidos, cuentos como dispositivos de Windows CE, enrutadores, puertas de enlace y consolas de videojuegos como Sony PlayStation 2 y PlayStation Portable. Hasta finales de 2006, también se usa en muchos de los productos informáticos de SGI. Implementaciones MIPS también se utilizaron por Digital Equipment Corporation, NEC, Pyramid Technology, Siemens Nixdorf, Tandem Computers y otros durante los años 1980 y 1990. Entre mediados y finales de 1990, se estima que uno de cada tres microprocesadores RISC fue una implementación MIPS.

ESTRUCTURA

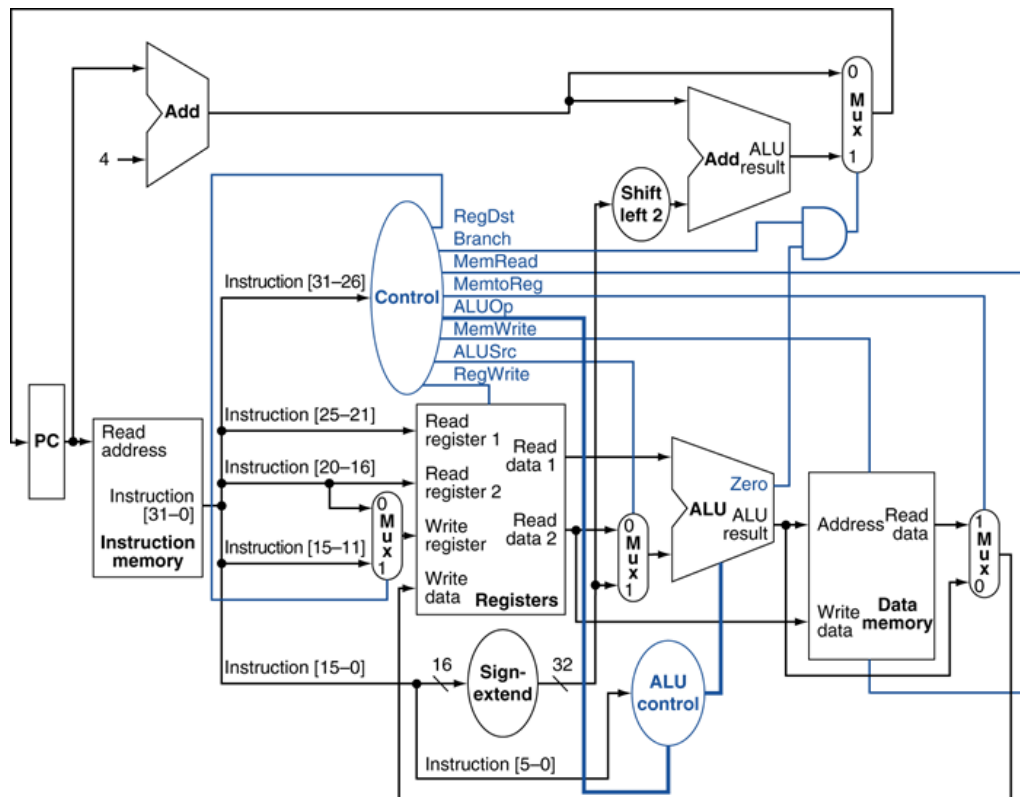



Casa abierta al tiempo

INSTRUCCIONES

- Tipo R

(shamt: shift amount en instrucciones de desplazamiento)

Cod. Op.	Registro fuente 1	Registro fuente 2	Registro destino		Funct
xxxxxxx	rs	rt	rd	shamt	funct
6	5	5	5	5	6
31-26	25-21	20-16	15-11	10-6	5-0

- Tipo I

(carga o almacenamiento, ramificación condicional, operaciones con inmediatos)

Cod. Op.	Registro base	Registro destino	Registro destino	Desplazamiento
xxxxxxx	rs	rt	rd	Offset
6	5	5	5	16
31-26	25-21	20-16	15-11	15-0

- Tipo J

(salto incondicional)

Cod. Op.	Dirección destino
xxxxxxx	target
6	26
31-26	20-16

REGISTROS

Nombre Registro	Número	Uso
zero	0	Constante 0
at	1	Reservado para el assembler
v0	2	Para evaluación de expresiones y retorno de resultados de la función
v1	3	
a0	4	Argumento1
a1	5	Argumento 2
a2	6	Argumento 3
a3	7	Argumento 4
t0	8	Temporal (no se preserva a través de los llamados)
t1	9	Temporal (no se preserva a través de los llamados)





Casa abierta al tiempo

t2	10	Temporal (no se preserva a través de los llamados)
t3	11	Temporal (no se preserva a través de los llamados)
t4	12	Temporal (no se preserva a través de los llamados)
t5	13	Temporal (no se preserva a través de los llamados)
t6	14	Temporal (no se preserva a través de los llamados)
t7	15	Temporal (no se preserva a través de los llamados)
s0	16	Temporal que debe preservarse entre llamados a funciones
s1	17	Temporal que debe preservarse entre llamados a funciones
s2	18	Temporal que debe preservarse entre llamados a funciones
s3	19	Temporal que debe preservarse entre llamados a funciones
s4	20	Temporal que debe preservarse entre llamados a funciones
s5	21	Temporal que debe preservarse entre llamados a funciones
s6	22	Temporal que debe preservarse entre llamados a funciones
s7	23	Temporal que debe preservarse entre llamados a funciones
t8	24	Temporal (no se preserva a través de los llamados)
t9	25	Temporal (no se preserva a través de los llamados)
k0	26	Reservado para el núcleo del sistema operativo
k1	27	Reservado para el núcleo del sistema operativo
gp	28	Puntero al área global de datos
sp	29	Puntero al tope de la pila. Stack pointer
fp	30	Puntero a zona de variables en la pila. Frame pointer
ra	31	Dirección de retorno (usado en invocaciones a funciones)





DESARROLLO

Control_alu.vhd	
<pre>library IEEE; use IEEE.STD_LOGIC_1164.all; entity control_alu is port(ALUOp: in std_logic_vector(1 downto 0); FuncCode: in std_logic_vector(5 downto 0); ALUCtl: out std_logic_vector(3 downto 0)); end control_alu; architecture estructural of control_alu is begin ALUCtl <= "0010" when ALUOp(1) = '0' and ALUOp(0) = '0' else "0110" when ALUOp(1) = '0' and ALUOp(0) = '1' else "0010" when ALUOp(1) = '1' and ALUOp(0) = '0' and FuncCode(3) = '0' and FuncCode(2) = '0' and</pre>	<pre>FuncCode(1) = '0' and FuncCode(0) = '0' else "0110" when ALUOp(1) = '1' and FuncCode(3) = '0' and FuncCode(2) = '0' and FuncCode(1) = '1' and FuncCode(0) = '0' else "0000" when ALUOp(1) = '1' and ALUOp(0) = '0' and FuncCode(3) = '0' and FuncCode(2) = '1' and FuncCode(1) = '0' and FuncCode(0) = '0' else "0001" when ALUOp(1) = '1' and ALUOp(0) = '0' and FuncCode(3) = '0' and FuncCode(2) = '1' and FuncCode(1) = '0' and FuncCode(0) = '1' else "0111" when ALUOp(1) = '1' and FuncCode(3) = '1' and FuncCode(2) = '0' and FuncCode(1) = '1' and FuncCode(0) = '0'; end estructural;</pre>

Control_unit.vhd	
<pre>--Unidad de control MIPS library IEEE; use IEEE.STD_LOGIC_1164.all; entity control_unit is port(op : in std_logic_vector(5 downto 0); RegDst:out std_logic; ALUSrc:out std_logic;</pre>	<pre>downto 0); begin ctrl_word <= "100100010" when op = "000000" else --instrucciones Type-R "011110000" when op = "100011" else --lw :0x23 "X1X001000" when op = "101011" else --sw :0x2B</pre>





Casa abierta al tiempo

<pre> x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", x"00000000", </pre>	<pre> RD2<=data_mem(to_integer(unsigned(RR2))); process(RegWrite) begin if (RegWrite='1') then data_mem(to_integer(unsigned(Write_ Register)))<=Write_Data; end if; end process; end Behavioral; </pre>
--	---

Registrer_File_v2.vhd	
<pre> library ieee; use ieee.std_logic_1164.all; entity Register_File is port (clk: in std_logic; reset: in std_logic; RegWrite:in std_logic; --señal de control RR1: in std_logic_vector (4 downto 0); --numero de registro 1 RR2: in std_logic_vector (4 downto 0); --numero de registro 2 Write_Register: in std_logic_vector (4 downto 0); Write_Data: in std_logic_vector (31 downto 0); --En el anterior numero guardar los 8 bytes de esta entrada RD1: out std_logic_vector (31 downto 0); --Salida de 32 bits. RD2: out std_logic_vector (31 downto 0); --Salida de 32 bits end Register_File; </pre>	<pre> std_logic_vector(31 downto 0); reset: in std_logic); end component re_hab_buff; end structural ; signal decoderRW_d_data: std_logic_vector(31 downto 0); signal decoderA_d_data: std_logic_vector(31 downto 0); signal decoderB_d_data: std_logic_vector(31 downto 0); begin decoderRW : dec5a32 port map(a => Write_Register, d => decoderRW_d_data, e => RegWrite); decoderA : dec5a32 port map(a => RR1, d => decoderA_d_data, e => '1' </pre>





Casa abierta al tiempo

<pre> architecture structural of Register_File is component dec5a32 port (a: in std_logic_vector(4 downto 0); e: in std_logic; d: out std_logic_vector(31 downto 0)); end component dec5a32; component re_hab_buff port(data_in: in std_logic_vector(31 downto 0); eBusA: in std_logic; eBusB: in std_logic; e: in std_logic; clk: in std_logic; dataBusA_out: out std_logic_vector(31 downto 0); dataBusB_out: out </pre>	<pre>); decoderB : dec5a32 port map(a => RR2, d => decoderB_d_data, e => '1'); alus : for i in 0 to 31 generate regis0_31 : re_hab_buff port map(data_in => Write_Data, eBusA => decoderA_d_data(i), eBusB => decoderB_d_data(i), e => decoderRW_d_data(i), clk => clk, dataBusA_out => RD1, dataBusB_out => RD2, reset => reset); end generate ; </pre>
---	--

Data_memory.vhd	
<pre> library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all; entity data_memory is port(clk, MemRead, MemWrite : in std_logic; address : in std_logic_vector(31 downto 0); datain : in std_logic_vector(31 downto 0); dataout : out std_logic_vector(31 downto 0)); end data_memory; </pre>	<pre> memDatos(to_integer(unsigned(address))+2) <= datain(15 downto 8); memDatos(to_integer(unsigned(address))+3) <= datain(7 downto 0); end if; end if; end process; --Asynchronous reading dataout(31 downto 24) <= memDatos(to_integer(unsigned(address s))) when MemRead = '1' else (others => 'Z'); </pre>





Casa abierta al tiempo

<pre> architecture behavioral of data_memory is type tipoRAM is array(0 to 255) of std_logic_vector(7 downto 0); signal memDatos : tipoRAM; begin process(clk) begin if rising_edge(clk) then if MemWrite = '1' then memDatos(to_integer(unsigned(address))) <= datain(31 downto 24); memDatos(to_integer(unsigned(address))+1) <= datain(23 downto 16); </pre>	<pre> dataout(23 downto 16) <= memDatos(to_integer(unsigned(address s))+1) when MemRead = '1' else (others => 'Z'); dataout(15 downto 8) <= memDatos(to_integer(unsigned(address s))+2) when MemRead = '1' else (others => 'Z'); dataout(7 downto 0) <= memDatos(to_integer(unsigned(address s))+3) when MemRead = '1' else (others => 'Z'); end behavioral; </pre>
--	---

Instruction_memory.vhd	
<pre> library ieee; use ieee.std_logic_1164.all; entity instruction_memory is port (addr: in std_logic_vector(31 downto 0); instruction: out std_logic_vector(31 downto 0)); end instruction_memory; architecture structural of instruction_memory is component dec5a32 port (a: in std_logic_vector(4 downto 0); e: in std_logic; d: out std_logic_vector(31 downto 0)); </pre>	<pre> dec_line(7) or dec_line(11) or dec_line(12) or dec_line(16); instruction(16) <= dec_line(0) or dec_line(2) or dec_line(3) or dec_line(5) or dec_line(7) or dec_line(8) or dec_line(9) or dec_line(13) or dec_line(16); instruction(15) <= dec_line(2) or dec_line(10) or dec_line(11) or dec_line(15); instruction(14) <= dec_line(3) or dec_line(5) or dec_line(7) or dec_line(8) or dec_line(10) or dec_line(12) or dec_line(13) or dec_line(15); instruction(13) <= dec_line(10) or dec_line(15); instruction(12) <= dec_line(2) or dec_line(7) or dec_line(10) or </pre>





Casa abierta al tiempo

<pre> end component dec5a32; signal dec_line: std_logic_vector(31 downto 0); begin decoder5x32_u: dec5a32 port map(a => addr(6 downto 2), d => dec_line, e => '1'); --TODO: Make the generation of decoder lines automatically instruction(31) <= dec_line(0) or dec_line(1) or dec_line(16); instruction(30) <= '0'; instruction(29) <= dec_line(16); instruction(28) <= dec_line(4) or dec_line(6) or dec_line(10) or dec_line(15); instruction(27) <= dec_line(0) or dec_line(1) or dec_line(16); instruction(26) <= dec_line(0) or dec_line(1) or dec_line(16); instruction(25) <= dec_line(14); instruction(24) <= dec_line(7) or dec_line(8) or dec_line(9) or dec_line(13); instruction(23) <= '0'; instruction(22) <= dec_line(7) or dec_line(14); instruction(21) <= dec_line(8) or dec_line(10) or dec_line(15); instruction(20) <= dec_line(0) or dec_line(1) or dec_line(2) or dec_line(3) or dec_line(5) or dec_line(7) or dec_line(8) or dec_line(13) or dec_line(16); instruction(19) <= dec_line(9) or dec_line(11) or dec_line(12) or dec_line(14); </pre>	<pre> dec_line(11) or dec_line(12) or dec_line(15); instruction(11) <= dec_line(2) or dec_line(5) or dec_line(8) or dec_line(9) or dec_line(10) or dec_line(11) or dec_line(14) or dec_line(15); instruction(10) <= dec_line(10) or dec_line(15); instruction(9) <= dec_line(10) or dec_line(15); instruction(8) <= dec_line(10) or dec_line(15); instruction(7) <= dec_line(10) or dec_line(15); instruction(6) <= dec_line(10) or dec_line(15); instruction(5) <= dec_line(2) or dec_line(3) or dec_line(5) or dec_line(7) or dec_line(8) or dec_line(9) or dec_line(10) or dec_line(11) or dec_line(12) or dec_line(13) or dec_line(14) or dec_line(15); instruction(4) <= dec_line(10) or dec_line(15); instruction(3) <= dec_line(4) or dec_line(9) or dec_line(10) or dec_line(14) or dec_line(16); instruction(2) <= dec_line(1) or dec_line(2) or dec_line(3) or dec_line(5) or dec_line(10) or dec_line(11) or dec_line(12) or dec_line(15); instruction(1) <= dec_line(6) or dec_line(9) or dec_line(14); instruction(0) <= dec_line(2) or dec_line(3) or dec_line(4) or dec_line(5) or dec_line(11) or dec_line(15); </pre>
---	--





Casa abierta al tiempo

instruction(18) <= '0'; instruction(17) <= dec_line(1) or	end structural ; -- structural
--	--------------------------------

alu32bits.vhd	
library IEEE; use IEEE.std_logic_1164.ALL; use ieee.numeric_std.all; entity alu32bits is port(entrada1:in std_logic_vector(31 downto 0); entrada2:in std_logic_vector(31 downto 0); control:in std_logic_vector (3 downto 0); result: out std_logic_vector(31 downto 0); zero:out std_logic); end alu32bits; architecture behavioral of alu32bits is begin result<=std_logic_vector(signed(entrada1)+signed(entrada2))when(control="0010")else std_logic_vector(signed(entrada1)-signed(entrada2))when(control="0110") 	else (entrada1) and (entrada2)when(control="0000")else (entrada1) or (entrada2)when(control="0001")else "00000000000000000000000000000000 01" when (control="0111" and entrada1<entrada2) else "00000000000000000000000000000000 00" when (control="0111"); zero<= '1' when (std_logic_vector(signed(entrada1)) = std_logic_vector(signed(entrada2)) and control="0110")else '1' when (std_logic_vector(signed(entrada1)) = std_logic_vector(-signed(entrada2)) and control="0010")else '1' when (control="0110")else '0'; end behavioral;

Processor.vhd	
library ieee; use ieee.std_logic_1164.all;	signal dtadm:std_logic_vector(31 downto 0);





Casa abierta al tiempo

<pre> entity processor is port (clock: in std_logic; reset: in std_logic); end processor; architecture structural of processor is component datapath is port (data_in: in std_logic_vector(31 downto 0); instruction: in std_logic_vector(25 downto 0); --RegDst, ALUSrc, MemToReg, RegWrite, PCSrc ctrlword: in std_logic_vector(4 downto 0); alu_code: in std_logic_vector(3 downto 0); data_out, mem_addr: out std_logic_vector(31 downto 0); instr_addr: out std_logic_vector(31 downto 0); clock, reset: in std_logic); end component datapath; component instruction_memory port (addr: in std_logic_vector(31 downto 0); instruction: out std_logic_vector(31 downto 0)); end component instruction_memory; component data_memory port(clk, MemRead, MemWrite : in std_logic; address : in std_logic_vector(31 downto 0); </pre>	<pre> signal dpadm:std_logic_vector(31 downto 0); signal cablememread:std_logic; signal cablememwrite:std_logic; signal aluopc:std_logic_vector (1 downto 0); --signal MemRead, MemWrite: std_logic; --signal initial_data, data, initial_addr, address: std_logic_vector(31 downto 0); --signal clock: std_logic := '0'; --signal reset: std_logic := '1'; --signal finish_flag: boolean := false; --signal initial_complete: boolean := false; --signal instruction_addr, instruction: std_logic_vector(31 downto 0); --RegDst, ALUSrc, MemToReg, RegWrite, MemRead, MemWrite, PCSrc, ALUOp1 y ALUOp0 begin --MemWrite <= '1' when initial_complete = false else unidadctrl_dataMemo_MemWrite; --MemRead <= '0' when initial_complete = false else unidadctrl_dataMemo_MemRead; -- data <= initial_data when initial_complete = false else ruta_dataMemo_data_out; -- address <= initial_addr when initial_complete = false else ruta_dataMemo_addresRes; memoriainstrucciones: instruction_memory port map(addr => direccion1, instruction => instruccion); unioncondatapath : datapath </pre>
--	--





Casa abierta al tiempo

<pre> datain : in std_logic_vector(31 downto 0); dataout : out std_logic_vector(31 downto 0)); end component data_memory; component control_unit port (op : in std_logic_vector(5 downto 0); RegDst:out std_logic; ALUSrc:out std_logic; MemToReg:out std_logic; RegWrite : out std_logic; MemRead, MemWrite, Branch : out std_logic; ALUOp : out std_logic_vector(1 downto 0)); end component control_unit; component control_alu port (ALUOp: in std_logic_vector(1 downto 0); FuncCode: in std_logic_vector(5 downto 0); ALUCtl: out std_logic_vector(3 downto 0)); end component control_alu; signal salidamemo:std_logic_vector(31 downto 0); signal instruccion:std_logic_vector(31 downto 0); signal palabracontrol:std_logic_vector(4 downto 0); signal salidaalucontrol:std_logic_vector(3 downto 0); </pre>	<pre> port map(clock => clock, reset => reset, data_in => salidamemo, instruction =>instruccion(25 downto 0), ctrlword => palabracontrol, alu_code => salidaalucontrol, mem_addr => dtadm, data_out => dpadm, instr_addr => direccion1); memoriadedatos : data_memory port map(clk => clock, --MemRead => MemRead, MemRead => cablememread, --MemWrite => MemWrite, MemWrite => cablememwrite, --address => address, address => dtadm, --datain => data, datain => dpadm, dataout => salidamemo); unidadedecontrol : control_unit port map(op => instruccion(31 downto 26), RegDst => palabracontrol(4), ALUSrc => palabracontrol(3), MemToReg => palabracontrol(2), RegWrite => palabracontrol(1), MemRead => cablememread, MemWrite => cablememwrite, Branch => palabracontrol(0), ALUOp => aluopc(1 downto 0)); alucontrol : control_alu port map(ALUOp => aluopc, FuncCode => instruccion(5 downto 0), ALUCtl => salidaalucontrol); </pre>
---	--





Casa abierta al tiempo

signal direccion1:std_logic_vector(31 downto 0);	end structural ; -- structural
---	--------------------------------

datapath.vhd	
<pre> library ieee; use ieee.std_logic_1164.all; entity datapath is port (data_in: in std_logic_vector(31 downto 0); instruction: in std_logic_vector(25 downto 0); --RegDst, ALUSrc, MemToReg, RegWrite, Branch ctrlword: in std_logic_vector(4 downto 0); alu_code: in std_logic_vector(3 downto 0); data_out, mem_addr: out std_logic_vector(31 downto 0); instr_addr: out std_logic_vector(31 downto 0); clock, reset: in std_logic) ; end datapath; architecture structural of datapath is component Register_File port (clk: in std_logic; reset: in std_logic; RegWrite:in std_logic; --señal de control RR1: in std_logic_vector (4 downto 0); --numero de registro 1 RR2: in std_logic_vector (4 downto 0); --numero de registro 2 Write_Register: in std_logic_vector (4 downto 0); </pre>	<pre> signal salida2r:std_logic_vector(31 downto 0); signal se_a_sll2:std_logic_vector(31 downto 0); signal sll2_a_ADDALU:std_logic_vector(31 downto 0); signal muxaalui:std_logic_vector(31 downto 0); signal rai:std_logic_vector(31 downto 0); signal aluaalu:std_logic_vector(31 downto 0); signal cablezero:std_logic; signal addamux:std_logic_vector(31 downto 0); signal salidapcaux:std_logic_vector(31 downto 0); signal retorno:std_logic_vector (31 downto 0); signal compuertaand:std_logic; begin primermux : mux5bits port map(entrada1 => instruction(20 downto 16), entrada2 => instruction(15 downto 11), sel => ctrlword(4), salida => muxaregistro); archivoderegistros: Register_File port map(RegWrite=>ctrlword(1), RR1=> instruction (25 downto 21), </pre>





Casa abierta al tiempo

<p>Write_Data: in std_logic_vector (31 downto 0); --En el anterior numero guardar los 8 bytes de esta entrada</p> <p>RD1: out std_logic_vector (31 downto 0); --Salida de 32 bits.</p> <p>RD2: out std_logic_vector (31 downto 0)); --Salida de 32 bits.</p> <p>end component Register_File;</p> <p>component alu32bits</p> <p>port(</p> <p> entrada1:in std_logic_vector(31 downto 0);</p> <p> entrada2:in std_logic_vector(31 downto 0);</p> <p> control:in std_logic_vector (3 downto 0);</p> <p> result: out std_logic_vector(31 downto 0);</p> <p> zero:out std_logic</p> <p>);</p> <p>end component alu32bits;</p> <p>component mux5bits</p> <p>port(</p> <p> entrada1: in std_logic_vector(4 downto 0);</p> <p> entrada2: in std_logic_vector(4 downto 0);</p> <p> sel: in std_logic;</p> <p> salida: out std_logic_vector(4 downto 0)</p> <p>);</p> <p>end component mux5bits;</p> <p>component mux32bits</p> <p>port(</p> <p> entrada1: in std_logic_vector(31 downto 0);</p> <p> entrada2: in std_logic_vector(31 downto 0);</p> <p> sel: in std_logic;</p>	<p>RR2=> instruction (20 downto 16),</p> <p>Write_Register=>muxaregistro,</p> <p>Write_Data=>cablememreg,</p> <p>RD1=>salida1r,</p> <p>RD2=>salida2r,</p> <p>clk=>clock,</p> <p>reset=>reset</p> <p>);</p> <p>extensordesigno:sign_ext</p> <p>port map(</p> <p> entrada16=>instruction(15 downto 0),</p> <p> salida32=>se_a_sll2</p> <p>);</p> <p>shiftright:sll2</p> <p>port map(</p> <p> entrada=>se_a_sll2,</p> <p> salida=>sll2_a_ADDALU</p> <p>);</p> <p>muxdespuesregistro:mux32bits</p> <p>port map(</p> <p> entrada1=>salida2r,</p> <p> entrada2=>se_a_sll2,</p> <p> sel=>ctrlword(3),</p> <p> salida=>muxaalui</p> <p>);</p> <p>aluimportante: alu32bits</p> <p>port map(</p> <p> entrada1=>salida1r,</p> <p> entrada2=>muxaalui,</p> <p> control=>alu_code,</p> <p> result=>rai,</p> <p> zero=>cablezero</p> <p>);</p> <p>muxsalidamemoria:mux32bits</p> <p>port map(</p> <p> entrada1=>rai,</p> <p> entrada2=>data_in,</p> <p> sel=>ctrlword(2),</p> <p> salida=>cablememreg</p>
---	--





Casa abierta al tiempo

<pre> salida: out std_logic_vector(31 downto 0)); end component mux32bits; component sll2 port(entrada: in std_logic_vector(31 downto 0); salida: out std_logic_vector(31 downto 0)); end component sll2; component sign_ext port(entrada16: in std_logic_vector(15 downto 0); salida32: out std_logic_vector(31 downto 0)); end component sign_ext; component pc_aux port(data_in: in std_logic_vector(31 downto 0); e: in std_logic; clk: in std_logic; data_out: out std_logic_vector(31 downto 0); reset: in std_logic); end component pc_aux; signal vacio: std_logic; signal muxregistro:std_logic_vector(4 downto 0); signal cablememreg:std_logic_vector(31 downto 0); signal salida1r:std_logic_vector(31 downto 0); </pre>	<pre>); sumador4:alu32bits port map(entrada1=>x"00000004", entrada2=>salidapcaux, control=>"0010", result=>aluaalu, zero=>vacio); sumadorsig:alu32bits port map(entrada1=>aluaalu, entrada2=>sll2_a_ADDALU, control=>"0010", result=>addamux, zero=>vacio); muxpc: mux32bits port map(entrada1=>aluaalu, entrada2=>addamux, sel=>compuertaand, salida=>retorno); pc_pc : pc_aux port map(data_in => retorno, e => '1', clk => clock, data_out => salidapcaux, reset => reset); instr_addr <= salidapcaux; data_out <= salida2r; mem_addr <= rai; compuertaand<=ctrlword(0) and cablezero; end structural ; -- structural </pre>
--	---





re_hab.vhd	
<pre>library ieee; use ieee.std_logic_1164.all; entity re_hab is port(data_in: in std_logic_vector(31 downto 0); e: in std_logic; clk: in std_logic; data_out: out std_logic_vector(31 downto 0); reset: in std_logic);</pre>	<pre>end re_hab; architecture behavioral of re_hab is begin process(clk) begin if clk'event and clk='1' then if (reset = '1') then data_out <= (others => '0'); elsif e='1' then data_out <= data_in; end if; end if; end process; end behavioral;</pre>

re_hab_buff.vhd	
<pre>library ieee; use ieee.std_logic_1164.all; entity re_hab_buff is port (data_in: in std_logic_vector(31 downto 0); eBusA: in std_logic; eBusB: in std_logic; e: in std_logic; clk: in std_logic; dataBusA_out: out std_logic_vector(31 downto 0); dataBusB_out: out std_logic_vector(31 downto 0); reset: in std_logic); end re_hab_buff;</pre>	<pre>data_out: out std_logic_vector(31 downto 0); reset: in std_logic); end component re_hab; signal re_buff: std_logic_vector(31 downto 0); signal busA: std_logic_vector(31 downto 0); signal busB: std_logic_vector(31 downto 0); begin regi : re_hab port map(data_in => data_in, reset => reset,</pre>





Casa abierta al tiempo

<pre> architecture structural of re_hab_buff is component tri_state_buff --Buffer de tres estados port (data_in: in std_logic_vector(31 downto 0); data_out: out std_logic_vector(31 downto 0); en_buff: in std_logic) ; end component tri_state_buff; component re_hab port(data_in: in std_logic_vector(31 downto 0); e: in std_logic; clk: in std_logic; </pre>	<pre> clk => clk, e => e, data_out => re_buff); triSateBusA : tri_state_buff port map(data_in => re_buff, data_out => busA, en_buff => eBusA); triSateBusB : tri_state_buff port map(data_in => re_buff, data_out => busB, en_buff => eBusB); dataBusA_out <= busA; dataBusB_out <= busB; end structural ; -- structural </pre>
---	--

tri_state_buff.vhd	
<pre> library ieee; use ieee.std_logic_1164.all; entity tri_state_buff is port(data_in: in std_logic_vector(31 downto 0); data_out: out std_logic_vector(31 downto 0); en_buff: in std_logic); </pre>	<pre> end tri_state_buff; architecture behavioral of tri_state_buff is begin gen_buffer_array : for i in 0 to 31 generate data_out(i) <= data_in(i) when (en_buff = '1') else 'Z'; end generate; end behavioral; </pre>






RESULTADOS

Control_alutb.vhd	
<pre> library IEEE; use IEEE.STD_LOGIC_1164.all; entity control_alutb is end control_alutb; architecture behavioral of control_alutb is component control_alu port(ALUOp: in std_logic_vector(1 downto 0); FuncCode: in std_logic_vector(5 downto 0); ALUCtl: out std_logic_vector(3 downto 0)); end component; signal s_ap: std_logic_vector(1 downto 0); signal s_f: std_logic_vector(5 downto 0); signal s_a: std_logic_vector(3 downto 0); begin prueba: control_alu port map(ALUOp=>s_ap,</pre>	<pre> FuncCode=>s_f, ALUCtl=>s_a); process begin s_ap <= "00"; s_f<="000000"; wait for 10 ns; s_f<="000001" ; wait for 10 ns; s_ap <= "01"; s_f<="000000"; wait for 10 ns; s_ap <= "10"; s_f<="100000"; wait for 10 ns; s_f<="100010"; wait for 10 ns; s_f<="100100"; wait for 10 ns; s_f<="100101"; wait for 10 ns; s_f<="101010"; wait for 10 ns; wait; end process; end behavioral;</pre>





Casa abierta al tiempo

 


Control_unit_tb.vhd	
<pre>library IEEE; use IEEE.STD_LOGIC_1164.all; entity control_unit_tb is end control_unit_tb; architecture behavioral of control_unit_tb is component control_unit port(op : in std_logic_vector(5 downto 0); RegDst, ALUSrc, MemToReg, RegWrite : out std_logic; MemRead, MemWrite, Branch : out std_logic; ALUOp : out std_logic_vector(1 downto 0)); end component;</pre>	<pre>begin ctrl: control_unit port map(op => s_op, RegDst => s_RegDst, ALUSrc => s_ALUSrc, MemToReg => s_MemToReg, RegWrite => s_RegWrite, MemRead => s_MemRead, MemWrite => s_MemWrite, Branch => s_Branch, aluop => s_aluop); process begin s_op <= "100011"; wait for 80 ns; s_op <= "011011"; wait for 80 ns;</pre>





Casa abierta al tiempo

<pre>signal s_op: std_logic_vector(5 downto 0); signal s_RegDst: std_logic; signal s_ALUSrc: std_logic; signal s_MemToReg: std_logic; signal s_RegWrite: std_logic; signal s_MemRead: std_logic; signal s_MemWrite: std_logic; signal s_Branch: std_logic; signal s_aluop: std_logic_vector(1 downto 0);</pre>	<pre>s_op <= "000100"; wait for 80 ns; s_op <= "000000"; wait for 80 ns; s_op <= "101011"; wait for 80 ns; wait; end process; end behavioral;</pre>
--	---

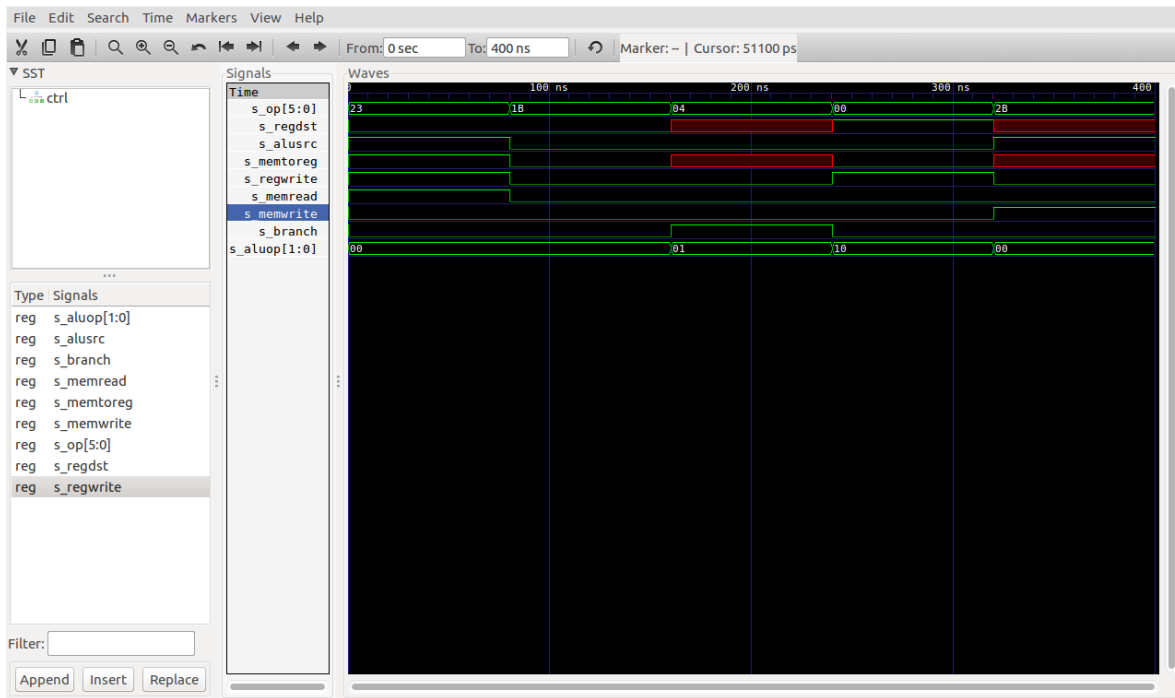




tbRegister_File.vhd	
<pre> library IEEE; use IEEE.STD_LOGIC_1164.all; entity tbRegister_File is end tbRegister_File; architecture behavioral of tbRegister_File is component Register_File port(RegWrite:in std_logic; --señal de control RR1: in std_logic_vector (4 downto 0); --numero de registro 1 RR2: in std_logic_vector (4 downto 0); --numero de registro 2 Write_Register: in std_logic_vector (4 downto 0); Write_Data: in std_logic_vector (31 downto 0); --En el anterior numero guardar los 8 bytes de esta entrada RD1: out std_logic_vector (31 downto 0); --Salida de 32 bits. RD2: out std_logic_vector (31 downto 0)); end component; signal s_Write_Data: std_logic_vector(31 downto 0); signal s_RD1: std_logic_vector(31 downto 0); signal s_RD2: std_logic_vector(31 downto 0); begin </pre>	<pre> rf: Register_File port map(RegWrite=>s_RegWrite, RR1=>s_RR1, RR2=>s_RR2, Write_Register=>s_Write_register, Write_Data=>s_Write_Data, RD1=>s_RD1, RD2=>s_RD2); process begin s_RegWrite <= '0'; wait for 2 ns; s_RegWrite <= '1'; s_RR1<="01000"; s_RR2<="00010"; s_Write_Register<="00010"; s_Write_Data<="11111111111111111111 1111111111111111"; wait for 8 ns; s_RegWrite<='0'; wait for 2 ns; s_RegWrite <= '1'; s_RR1<="01000"; s_RR2<="00010"; s_Write_Register<="01000"; s_Write_Data<="000000001111111111 1111111111111111"; wait for 8 ns; wait; end process; end behavioral; </pre>





Casa abierta al tiempo

 

Data_memorytb.vhd	
<pre>library IEEE; use IEEE.STD_LOGIC_1164.all; entity data_memorytb is end data_memorytb; architecture behavioral of data_memorytb is component data_memory port(clk, MemRead, MemWrite : in std_logic; address : in std_logic_vector(31 downto 0); datain : in std_logic_vector(31 downto 0); dataout : out std_logic_vector(31 downto 0)); end component;</pre>	<pre>s_clk<='0'; s_addr<=x"00000000"; s_MemRead<='0'; s_di<=x"FFFFFFFF"; s_MemWrite<='1'; wait for 10 ns; s_clk<='1'; wait for 10 ns; s_clk<='0'; s_MemRead<='1'; s_MemWrite<='0'; wait for 10 ns; s_clk<='1'; wait for 10 ns; s_MemRead<='0'; s_clk<='0'; s_MemWrite<='0'; s_addr<=x"00000004"; s_di<=x"ABABABAB"; wait for 10 ns; s_clk<='1';</pre>






Casa abierta al tiempo

```
signal s_addr: std_logic_vector(31
downto 0);
signal s_clk: std_logic;
signal s_MemRead: std_logic;
signal s_MemWrite: std_logic;
signal s_di: std_logic_vector(31
downto 0);
signal s_do: std_logic_vector(31
downto 0);
```

```
begin
  memoria: data_memory
  port map(
    address => s_addr,
    clk => s_clk,
    MemRead => s_MemRead,
    MemWrite => s_MemWrite,
    datain => s_di,
    dataout => s_do
  );
process
begin
```

```
wait for 10 ns;
s_clk<='0';
s_MemWrite<='1';
wait for 10 ns;
s_clk<='1';
wait for 10 ns;
s_clk<='0';
s_MemWrite<='0';
s_MemRead<='1';
s_addr<=x"00000008";
wait for 10 ns;
s_clk<='1';
s_MemRead<='1';
s_addr<=x"00000000";
wait for 10 ns;
s_clk<='0';
s_MemRead<='1';
s_addr<=x"00000004";
wait for 10 ns;
```
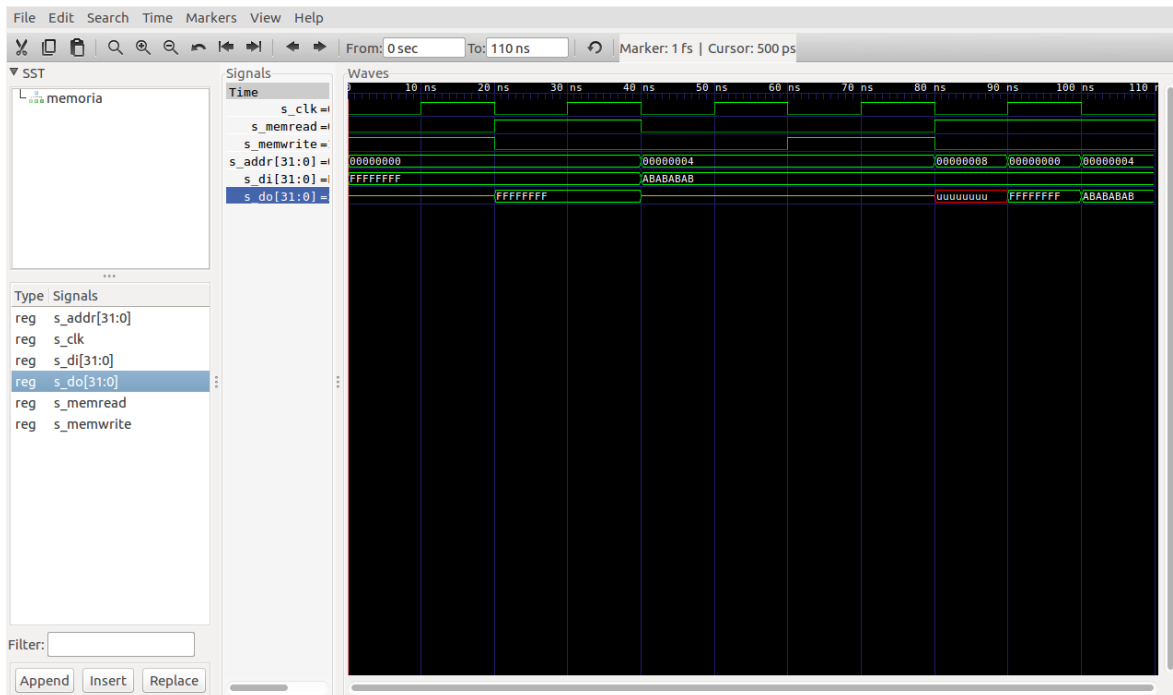
```
wait;
end process;
end behavioral;
```






Instruction_memorytb.vhd	
<pre>library ieee; use ieee.std_logic_1164.all; use ieee.math_real.all; use ieee.numeric_std.all; entity instruction_memorytb is end instruction_memorytb; architecture mixed of instruction_memorytb is component instruction_memory port (addr: in std_logic_vector(31 downto 0); instruction: out std_logic_vector(31 downto 0)); end component instruction_memory; signal s_addr: std_logic_vector(31 downto 0);</pre>	<pre>signal s_instruction: std_logic_vector(31 downto 0); begin rom: instruction_memory port map(addr => s_addr, instruction => s_instruction); stimuli : process begin for i in 0 to 31 loop s_addr <= std_logic_vector(to_unsigned(4*i, s_addr'length)); wait for 1 ns; end loop; wait; end process stimuli; -- stimuli end mixed ; -- mixed</pre>



Casa abierta al tiempo

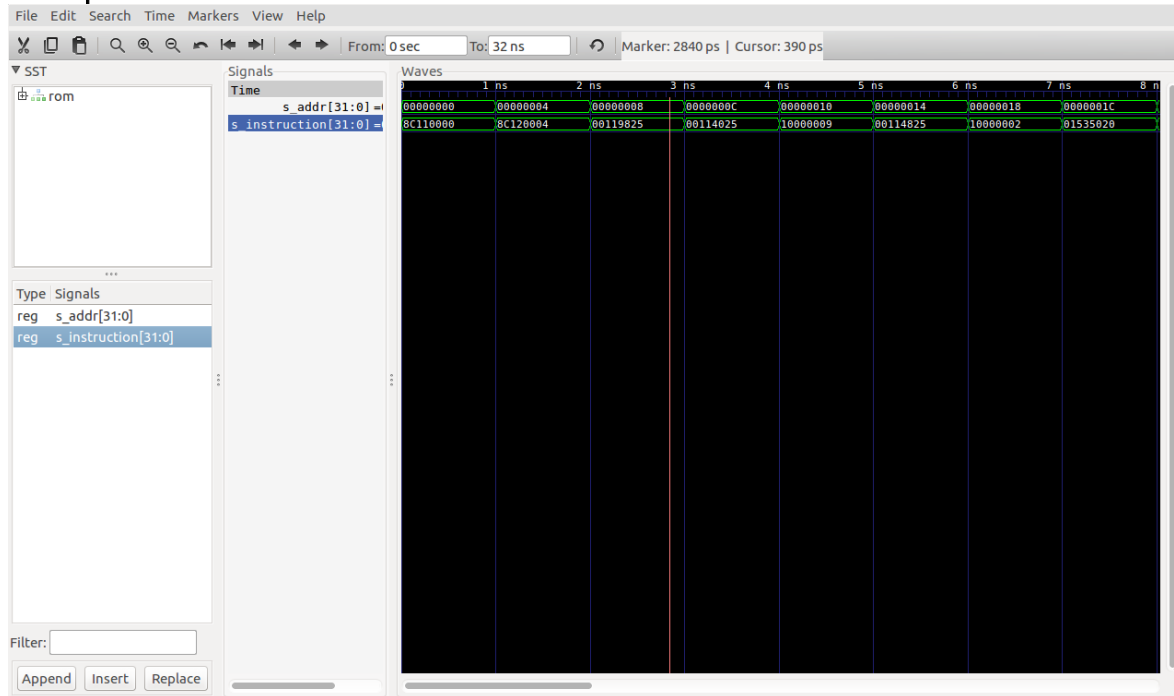

Tbalu32bits.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity tbalu32bits is
end tbalu32bits;

architecture behavioral of tbalu32bits is
    component alu32bits
    port(
        entrada1:in std_logic_vector(31
downto 0);
        entrada2:in std_logic_vector(31
downto 0);
        control:in std_logic_vector (3 downto
0);
        result: out std_logic_vector(31
downto 0);
        zero:out std_logic
    );
    end component;
```

```
        entrada2=>s_e2,
        control=>s_c,
        result=>s_r,
        zero=>s_z);

process
begin
    s_e1 <= x"00000005";
    s_e2 <= x"00000004";
    wait for 10 ns;
    s_c<="0111";
    wait for 10 ns;
    s_c<="0000";
    wait for 10 ns;
    s_c<="0001";
    wait for 10 ns;
    s_c<="0010";
    wait for 10 ns;
    s_c<="0110";
    wait for 10 ns;
```






Casa abierta al tiempo

```
signal s_e1: std_logic_vector(31
downto 0);
signal s_e2: std_logic_vector(31
downto 0);
signal s_c: std_logic_vector(3
downto 0);
signal s_r: std_logic_vector(31
downto 0);
signal s_z: std_logic;
```

```
begin
  prueba: alu32bits
  port map(
    entrada1=>s_e1,
```
 
```
s_e1 <= x"00000003";
s_e2 <= x"00000004";
wait for 10 ns;
s_c<="0111";
wait for 10 ns;
s_c<="0000";
wait for 10 ns;
s_c<="0001";
wait for 10 ns;
s_c<="0010";
wait for 10 ns;
s_c<="0110";
wait for 10 ns;
wait;
end process;
end behavioral; mixed
```





SIMULACIÓN FINAL Processor_testbench.vhd	
<pre>library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all; entity processor_testbench is end processor_testbench; architecture structural of processor_testbench is signal MemRead, MemWrite: std_logic; signal initial_data, data, initial_addr, address: std_logic_vector(31 downto 0); signal clock: std_logic := '0'; signal reset: std_logic := '1'; signal finish_flag: boolean := false; signal initial_complete: boolean := false; signal instr_addr, instruction_addr, instruction: std_logic_vector(31 downto 0); signal mem_data_out, mem_data_in, mem_data_addr: std_logic_vector(31 downto 0); --RegDst, ALUSrc, MemToReg, RegWrite, MemRead, MemWrite, PCSrc, ALUOp1 y ALUOp0 signal ctrlword: std_logic_vector(8 downto 0); signal alu_opcode: std_logic_vector(3 downto 0); component datapath is port (data_in: in std_logic_vector(31 downto 0); instruction: in std_logic_vector(25 downto 0);</pre>	<pre>ctrlword(3); MemRead <= '0' when initial_complete = false else ctrlword(4); data <= initial_data when initial_complete = false else mem_data_in; address <= initial_addr when initial_complete = false else mem_data_addr; datapath_unit: datapath port map(data_in => mem_data_out, instruction => instruction (25 downto 0), ctrlword(4) => ctrlword(8), --RegDest ctrlword(3) => ctrlword(7), --ALUSrc ctrlword(2) => ctrlword(6), -- MemToReg ctrlword(1) => ctrlword(5), -- RegWrite ctrlword(0) => ctrlword(2), --Branch alu_code => alu_opcode, data_out => mem_data_in, mem_addr => mem_data_addr, instr_addr => instruction_addr, clock => clock, reset => reset); alu_control_unit: control_alu port map(ALUOp => ctrlword(1 downto 0), FuncCode => instruction(5 downto 0), ALUCtl => alu_opcode); unidadcontrol: control_unit port map(op => instruction(31 downto 26), RegDst => ctrlword(8),</pre>





Casa abierta al tiempo

<pre> --RegDst, ALUSrc, MemToReg, RegWrite, branch ctrlword: in std_logic_vector(4 downto 0); alu_code: in std_logic_vector(3 downto 0); data_out, mem_addr: out std_logic_vector(31 downto 0); instr_addr: out std_logic_vector(31 downto 0); clock, reset: in std_logic); end component datapath; component instruction_memory port (addr: in std_logic_vector(31 downto 0); instruction: out std_logic_vector(31 downto 0)); end component instruction_memory; component data_memory port(clk, MemRead, MemWrite : in std_logic; address : in std_logic_vector(31 downto 0); datain : in std_logic_vector(31 downto 0); dataout : out std_logic_vector(31 downto 0)); end component data_memory; component control_unit port (op : in std_logic_vector(5 downto 0); RegDst, ALUSrc, MemToReg, RegWrite : out std_logic; MemRead, MemWrite, Branch : out std_logic; </pre>	<pre> ALUSrc => ctrlword(7), MemToReg => ctrlword(6), RegWrite => ctrlword(5), MemRead => ctrlword(4), MemWrite => ctrlword(3), Branch => ctrlword(2), ALUOp => ctrlword(1 downto 0)); instruction_memory_unit: instruction_memory port map(addr => instruction_addr, instruction => instruction); data_memory_unit: data_memory port map(clk => clock, MemRead => MemRead, MemWrite => MemWrite, address => address, datain => data, dataout => mem_data_out); clk_gen : process begin wait for 1 ns; clock <= not clock; if finish_flag = true then wait; end if; end process clk_gen; -- clk_gen reset_p : process begin wait for 4 ns; reset <= '0'; wait; end process reset_p; -- reset_p write_mem : process begin </pre>
---	--






Casa abierta al tiempo

<pre> ALUOp : out std_logic_vector(1 downto 0)); end component control_unit; component control_alu port (ALUOp : in std_logic_vector(1 downto 0); FuncCode : in std_logic_vector(5 downto 0); ALUCtl : out std_logic_vector(3 downto 0)); end component control_alu; begin MemWrite <= '1' when initial_complete = false else</pre>	<pre> initial_addr <= x"00000000"; initial_data <= x"00000001"; -- 1 wait for 2 ns; initial_addr <= x"00000004"; initial_data <= x"0000000a"; -- 1 wait for 2 ns; initial_complete <= true; wait; end process ; -- write_mem stimuli : process begin while initial_complete = false loop wait for 1 ns; end loop ; processing : while instruction /= x"00000000" loop wait for 1 ns; end loop ; -- processing finish_flag <= true; wait; end process stimuli; -- stimuli end structural ; -- structural</pre>
---	--





Casa abierta al tiempo

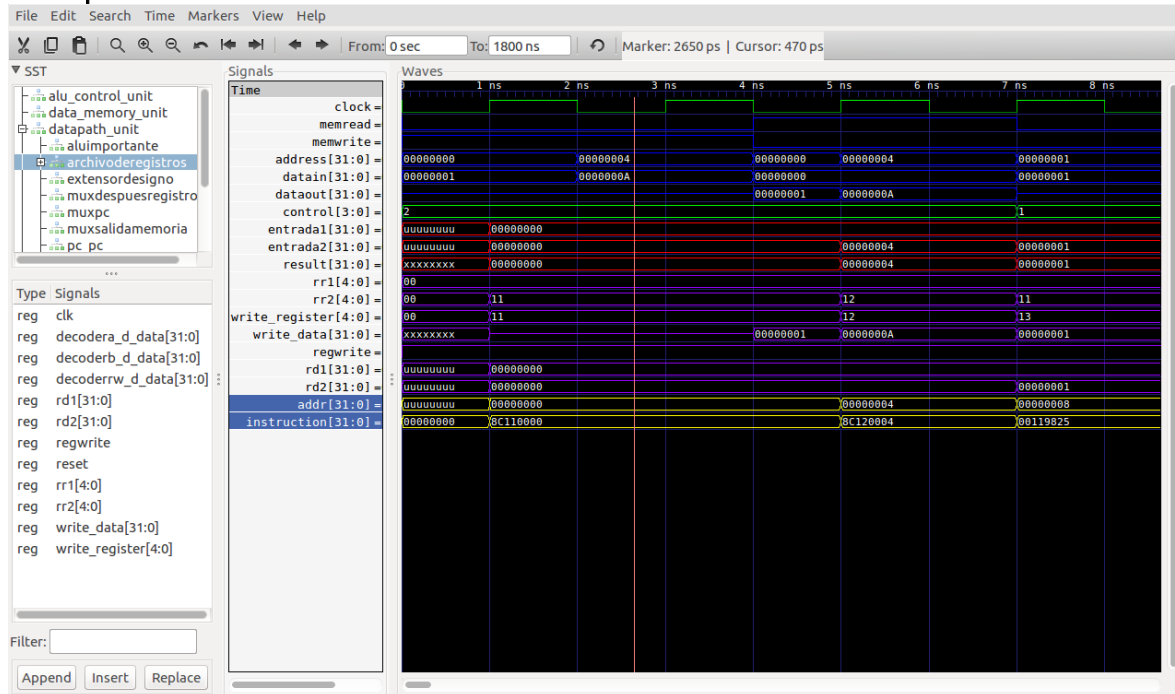

Conclusion

Para un programador sin mucha experiencia en lenguajes de descripción de hardware esto fue una travesía. Como se ha visto en clase la arquitectura MIPS en procesadores es ampliamente usada, mas en la década de los noventas. Su implementación en VHDL tiene su truco, como podemos observar muchos modulos están programados de manera “Behavioral” y otros “Structural” y esto tiene su razón de ser. A la hora del desarrollo y al evaluar cada modulo individualmente no tuve ningún problema, sin embargo a la hora de simular todo el procesador me enfrente a que no hay lo que tenia que hacer, las instrucciones no salían adecuadamente, dicho problema lo resolví pero ahora me enfrente a que mi Register_File no otorgaba los valores de salida, en el desarrollo se puede apreciar que hay dos Register_File, el primero programado de una manera similar a la Data Memory el siguiente Register_File_v2 programado de una manera más estructural. Aquí entra un aprendizaje de este proyecto, el “alto nivel” en VHDL a pesar de ser muy comodo no es lo más efectivo (al menos en este proyecto) ya que al desarrollar Register_File (y la ALU32bits) quise ahorrar tiempo programándolo de manera Funcional y no Estructural, debido a esto es que mis primeras simulaciones no prosperaron. Al investigar como hacer el Register_File me encuentro con modelos pensados en bajo nivel asi nace Register_File_v2 y gracias a la implementación de este es que la simulación corre.





Sin embargo me encuentro con otro contratiempo dentro de la simulación, las direcciones que entran a address de Data_Memory estaban incorrectas a lo que la ALU otorgaba y eso lo resolví modificando un cable mal conectado al MUX que recibe la salida del sign_extender. Es así como la simulación corre exitosamente, las instrucciones, las direcciones, entradas y salidas de diversos módulos corresponden con la instrucción entrante. En la captura de pantalla adjunte las señales de los módulos que considere más importantes en azul se encuentran las señales del data_memory, en rojo las señales de la ALU32bits, en morado las del Register_File y en amarillo las señales del PC_Aux. Es importante recalcar que la ALU32bits la deje en una programación "Comportamiento" ya que hace su labor correctamente sin embargo creo que sería mejor una programación del tipo Estructural como la del Register_File. En conclusión, al programar en VHDL un dispositivo como un procesador con cierta arquitectura es siempre mejor usar el modo Estructural para algunos módulos, el ganar tiempo programando el comportamiento de los módulos no es lo ideal aquí. Para finalizar aparte de la simulación final adjunte también la simulación de cada uno de los módulos individualmente, en el caso del Register_File deje la primera simulación ya que el funcionamiento del Register_File_v2 se veía en la simulación del procesador completo.

